

## EELE 461/561 – Digital System Design

### Module #2 – Interconnect Modeling with Lumped Elements

- **Topics**
  1. Modeling Techniques
  2. Impedance of Resistors, Capacitors and Inductors
- **Textbook Reading Assignments**
  1. 3.1-3.7
- **What you should be able to do after this module**
  1. Understand what a model is
  2. Describe the impedance of a Resistor, Capacitor, and Inductor



## Interconnect Modeling

- **Interconnect Modeling**
  - All interconnect can be described using the fundamentals of electromagnetic wave propagation given by Maxwell's equations.
  - However, it is impractical to use Maxwell's equations in real designs due to the time associated with the solutions.
  - Instead, we try to *Model* the performance of the interconnect using our basic circuit elements.
  - We use the word *Model* to describe the schematic of a circuit that mimics the electrical behavior of a physical structure.
  - A model not only gives us a gut feel, but it can be simulated with SPICE.
  - Since simulators only operate on ideal components, we need to construct our equivalent circuit model using
    - i.e., Resistors, Capacitors, Inductors, and Transmission Lines



## Interconnect Modeling

- **Interconnect Modeling**
  - The accuracy of a model can be increased by using more circuit elements.
  - However, more circuit elements cause the simulation to run slower.
  - As a result, we want a *Model* that is:
    - 1) Accurate enough for our application
    - 2) Not overly complex resulting in longer-than-necessary simulation times
  - A model is also accurate over a finite frequency range. We call this the:  
*"Bandwidth of the Model"*
  - The model may be accurate over its bandwidth, but may give inaccurate results above its BW.
  - We need to make sure that our model has sufficient bandwidth to accurately predict the behavior for all spectral content in our system.
  - Again, the more circuit elements in the model, the higher range of frequency that the model can cover.



## Interconnect Modeling

- **Interconnect Modeling**
  - There are 4 ideal circuit elements that we use to describe a circuit's behavior:

<u>Lumped Elements</u>	<u>Distributed Elements</u>
Resistor (R) Capacitor (C) Inductor (L)	Transmission Line (T)
  - "Lumped" means there is no propagation time through the element
  - "Distributed" means there **IS** propagation time through the element



## Impedance

- **Impedance**
  - In all cases, the most important electrical parameter of a system is its **Impedance**
  - Impedance is ALWAYS defined as:
$$Z = \frac{V}{I}$$
  - At first glance, this looks just like a resistor, but Impedance is the generic expression that includes time & frequency dependence.



## Impedance (R)

- **Z of a Resistor**
  - Resistance is the Ratio of DC Voltage to DC Current
  - The fundamental expression that describes the performance of a resistor is **Ohm's Law**:
$$V = I \cdot R$$
  - substituting this into the definition for Impedance, we can find  $Z_R$ 
$$Z_R = \frac{V}{I} = \frac{I \cdot R}{I} = R$$
$$Z_R = R$$
  - this is obvious, but one important takeaway is that an ideal resistor element has a fixed impedance that is **not dependent on frequency**



## Impedance (C)

### • Z of a Capacitor

- Capacitance is the Ratio of Charge stored between two conducting nodes to the voltage across the same nodes:

$$C = \frac{Q}{V}$$

- Large Capacitance means that more charge can be stored with less voltage.
- Physically, a capacitor is made of two plates separated by an insulating (dielectric) material.
  - Since the two plates are isolated, there is **NO DC Current**
  - if we inject charge suddenly on one of the capacitor nodes, the dielectric will polarize and cause charge to move on the opposite node. This instantaneous charge movement is **AC or transient current**.



## Impedance (C)

### • Z of a Capacitor

- If we look at the definition of Current, we can form a relationship for the behavior of a capacitor:

$$I = \frac{dQ}{dt}$$

- Let's rearrange our capacitor definition and then differentiate with respect to time:

$$C = \frac{Q}{V}$$

$$Q = CV$$

$$\frac{dQ}{dt} = C \frac{dV}{dt}$$

$$i_c = C \frac{dV}{dt}$$


- This is the fundamental expression that describes the behavior of a capacitor.



## Impedance (C)
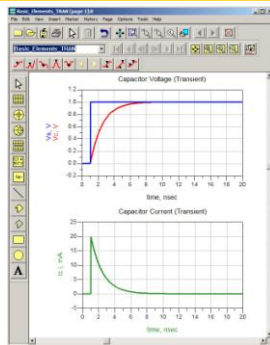
### • Z of a Capacitor

- This expression says that voltage cannot change instantaneously but current can.
- A small change in voltage will result in a large change in current.



## Impedance (C)

### • Z of a Capacitor

#### Time Domain

- if we look at the impedance of a capacitor in the time domain, we first remember that impedance is always  $V/I$

$$Z = \frac{V}{I} = - \frac{V}{C \frac{dV}{dt}}$$

- this expression that says:

- 1) when  $dV/dt$  is small (or DC), the capacitor impedance is HIGH
- 2) when  $dV/dt$  is large (or High Frequency), the capacitor impedance is LOW

- we conceptually say:

- 1) At DC, a capacitor looks like an **OPEN**.
- 2) At High Frequency, a capacitor looks like a **SHORT**.



## Impedance (C)

### • Z of a Capacitor

#### Time Domain

- let's represent our voltage in the time domain using sine waves:

$$V = V_0 \sin(\omega t)$$

- now let's derive the current of a capacitor using this voltage:

$$i_c = C \frac{dV}{dt} = C \frac{d(V_0 \sin(\omega t))}{dt}$$

$$i_c = \omega \cdot C \cdot V_0 \cos(\omega t)$$

- Now plugging into our Impedance expression for capacitance, we get:

$$Z_c = \frac{V}{I} = \frac{V_0 \sin(\omega t)}{\omega \cdot C \cdot V_0 \cos(\omega t)}$$

$$Z_c = \frac{1}{\omega \cdot C} \cdot \frac{\sin(\omega t)}{\cos(\omega t)}$$



## Impedance (C)

### • Z of a Capacitor

#### Time Domain

$$Z_c = \frac{1}{\omega \cdot C} \cdot \frac{\sin(\omega t)}{\cos(\omega t)}$$

- This expression tells us two important things:

- 1) The magnitude of the Impedance is:  $|Z_c| = \frac{1}{\omega \cdot C}$
- 2) The phase of the Impedance is:  $\text{ang}(Z_c) = -90^\circ$

- we say that the Voltage LAGS behind the Current in a capacitor by  $90^\circ$ , or "ICE"



## Impedance (C)

### • Z of a Capacitor


#### Frequency Domain

- In the frequency domain, we only have sine waves with Magnitude, Frequency, and Phase.
- We use a complex plane to represent the magnitude and phase with one complex quantity.
- On the complex plane, we represent a -90° phase using a -j
- Remember on the complex plane:

$$Z = a + jb$$

$$|Z| = \sqrt{a^2 + b^2}$$
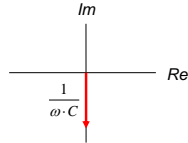
$$\text{ang}(Z) = \tan^{-1}\left(\frac{a}{b}\right)$$



## Impedance (C)


### • Z of a Capacitor

#### Frequency Domain

- The impedance of the capacitor can be expressed as:

$$Z_c = -j \cdot \left(\frac{1}{\omega \cdot C}\right)$$
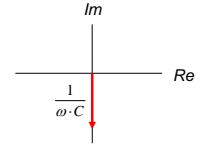
$$Z_c = \frac{1}{j\omega \cdot C} = \frac{1}{C \cdot s}$$



- Note that Impedance is a *complex quantity* and we define the *Complex Frequency* as  $s=j\omega$
- We call the Real part of Impedance **Resistance** and the Imaginary part **Reactance**.
- Since a capacitor only has an imaginary component, we can say that the Reactance is equal to the Impedance.

$$X_c = \frac{1}{C \cdot s} = Z_c$$



## Impedance (C)

### • Z of a Capacitor

#### Frequency Domain

- We typically get the most information from the magnitude of the impedance.

$$|Z_c| = \frac{1}{\omega \cdot C} = \frac{1}{2\pi \cdot f \cdot C}$$

- Note this shows an inverse relationship between Impedance and Frequency
- This verifies what we saw in the Time Domain:

- 1) At DC, a capacitor looks like an **OPEN**.
- 2) At High Frequency, a capacitor looks like a **SHORT**.




## Impedance (C)

### • Z of a Capacitor

#### Frequency Domain

$$|Z_c| = \frac{1}{2\pi \cdot f \cdot C}$$

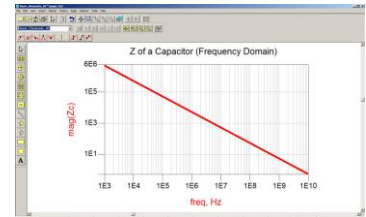

## Impedance (L)

### • Z of an Inductor

- Inductance is the ratio of Magnetic Flux to Current

$$L = \frac{\Phi}{I}$$

- Magnetic Flux is the number of B-field Lines around the conductor (units are Webers, Wb)
- Large Inductance means that more magnetic fields can be stored with less current.
- Physically, an inductor is a structure or material that can temporarily hold Magnetic field lines  
ex) a coil, or Ferroelectric material



## Impedance (L)

### • Z of an Inductor

- Faraday's Law of Induction states that the voltage induced from an inductor is:

$$V = \frac{d\Phi}{dt}$$

- Let's rearrange our inductance definition and then differentiate with respect to time:

$$L = \frac{\Phi}{I}$$

$$\Phi = L \cdot I$$

$$\frac{d\Phi}{dt} = L \frac{dI}{dt}$$

$$v_L = L \frac{dI}{dt}$$


- This is the fundamental expression that describes the behavior of an inductor.



## Impedance (L)

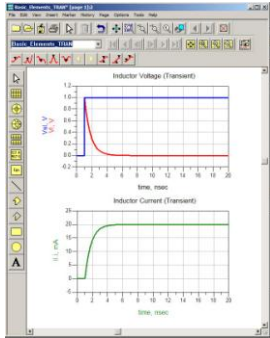**Z of an Inductor**

- This expression says that current cannot change instantaneously but voltage can.
- A small change in current will result in a large change in voltage.



## Impedance (L)

**Z of an Inductor**

Time Domain

- if we look at the impedance of an inductor in the time domain, we first remember that impedance is always  $V/I$

$$Z = \frac{V}{I} = \frac{L \cdot \frac{dI}{dt}}{I}$$

- this expression that says:

- 1) when  $dI/dt$  is small (or DC), the inductor impedance is LOW
- 2) when  $dI/dt$  is large (or High Frequency), the inductor impedance is HIGH

- we conceptually say:

- 1) At DC, an inductor looks like a **SHORT**.
- 2) At High Frequency, an inductor looks like an **OPEN**.



## Impedance (L)

**Z of an Inductor**

Time Domain

- let's represent our current in the time domain using sine waves:

$$I = I_0 \sin(\omega t)$$

- now let's derive the voltage of an inductor using this current:

$$v_L = L \frac{dI}{dt} = L \frac{d(I_0 \sin(\omega t))}{dt}$$

$$v_L = \omega \cdot L \cdot I_0 \cos(\omega t)$$

- Now plugging into our Impedance expression for inductance, we get:

$$Z_L = \frac{V}{I} = \frac{\omega \cdot L \cdot I_0 \cos(\omega t)}{I_0 \sin(\omega t)}$$

$$Z_L = \omega \cdot L \cdot \frac{\cos(\omega t)}{\sin(\omega t)}$$



## Impedance (L)

**Z of an Inductor**

Time Domain

$$Z_L = \omega \cdot L \cdot \frac{\cos(\omega t)}{\sin(\omega t)}$$

- This expression tells us two important things:

- 1) The magnitude of the Impedance is:  $|Z_L| = \omega \cdot L$
- 2) The phase of the Impedance is:  $\text{ang}(Z_L) = +90^\circ$

- we say that the Voltage LEADS the Current in an inductor by  $90^\circ$ , or "ELI"



## Impedance (L)

**Z of an Inductor**


Frequency Domain

- In the frequency domain, we only have sine waves with Magnitude, Frequency, and Phase.
- We use a complex plane to represent the magnitude and phase with one complex quantity.
- On the complex plane, we represent a  $+90^\circ$  phase using a  $+j$
- Remember on the complex plane:

$$Z = a + jb$$

$$|Z| = \sqrt{a^2 + b^2}$$
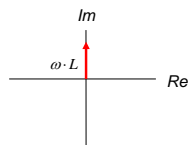
$$\text{ang}(Z) = \tan^{-1}\left(\frac{b}{a}\right)$$




## Impedance (L)

**Z of an Inductor**

Frequency Domain

- The impedance of the inductor can be expressed as:
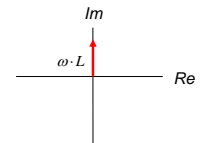
$$Z_L = j \cdot \omega \cdot L = s \cdot L$$



- Again, we call the Real part of Impedance **Resistance** and the Imaginary part **Reactance**.

- Since an inductor only has an imaginary component, we can say that the Reactance is equal to the Impedance.

$$X_L = s \cdot L = Z_L$$



## Impedance (L)

- **Z of an Inductor**

Frequency Domain

- In the Frequency Domain, the magnitude of the impedance is:

$$|Z_L| = \omega \cdot L = 2\pi \cdot f \cdot L$$

- Note this shows a linear relationship between Impedance and Frequency

- This verifies what we saw in the Time Domain:

- 1) At DC, an inductor looks like a **SHORT**.
- 2) At High Frequency, an inductor looks like an **OPEN**.



## Impedance (L)

- **Z of an Inductor**

Frequency Domain

$$|Z_L| = \omega \cdot L = 2\pi \cdot f \cdot L$$

