

• EELE 250 Practice Problems

• P2.57, P2.59, P2.91 <--note that these involve controlled source

• P3.26, P3.28, P3.48, P3.49

P2.57* First, we can write: $i_x = \frac{v_1 - v_2}{5}$.

Then, writing KCL equations at nodes 1 and 2, we have:

$$\frac{v_1}{10} + i_x = 1 \quad \text{and} \quad \frac{v_2}{20} + 0.5i_x - i_x = 0$$

Substituting for i_x and simplifying, we have

$$0.3v_1 - 0.2v_2 = 1$$

$$-0.1v_1 + 0.15v_2 = 0$$

Solving, we have $v_1 = 6$ and $v_2 = 4$.

Then, we have $i_x = \frac{v_1 - v_2}{5} = 0.4 \text{ A}$.

P2.59 First, we can write:

$$i_x = \frac{5i_x - v_2}{10}$$

Simplifying, we find $i_x = -0.2v_2$.

Then write KCL at nodes 1 and 2:


$$\frac{v_1 - 5i_x}{5} = 4 + 2 \quad \frac{v_2}{10} - i_x = -6$$

Substituting for i_x and simplifying, we have

$$v_1 + v_2 = 30 \quad \text{and} \quad 0.3v_2 = -6$$


which yield $v_1 = 50 \text{ V}$ and $v_2 = -20 \text{ V}$.

P2.91 Open-circuit conditions:

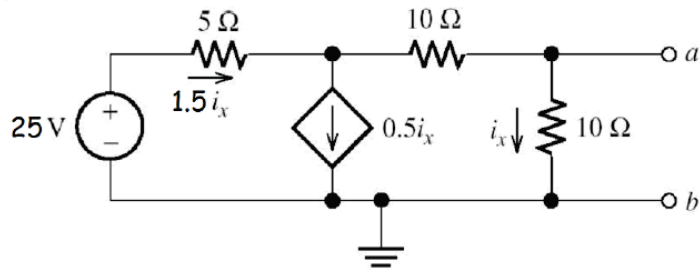


Using KVL, we have $25 = 5(1.5i_x) + 10i_x + 10i_x$. Solving, we find $i_x = 0.90909$ A and then we have $V_t = v_{oc} = 10i_x = 9.0909$ V.

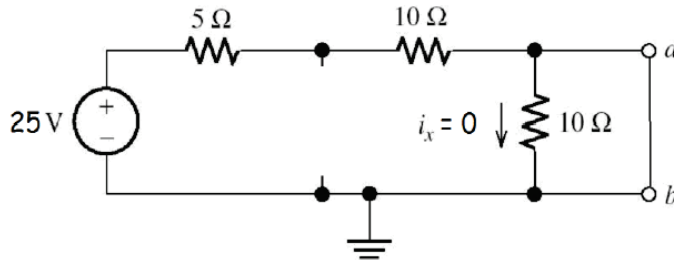Under short-circuit conditions, we have $i_x = 0$ and the controlled source becomes an open circuit:



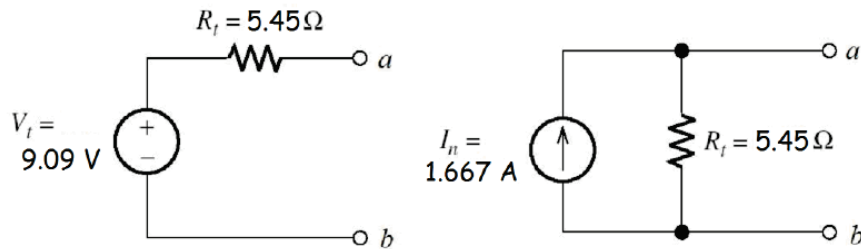$i_{sc} = \frac{25}{15} = 1.667$ A. Then, we have $R_t = v_{oc}/i_{sc} = 5.45 \Omega$. Thus, the equivalents are:



P3.26 (a) $C_{eq} = 3 + \frac{1}{1/2 + 1/1} + \frac{1}{1/2 + 1/(1+1)} = 4.667 \mu\text{F}$

(b) $C_{eq} = \frac{1}{1/(2+1) + 1/(4+2)} = 2 \mu\text{F}$

P3.28 $C_{eq} = \frac{1}{1/C_1 + 1/C_2} = 6 \mu\text{F}$

The charges stored on each capacitor and on the equivalent capacitance are equal because the current through each is the same.

$$Q = C_{eq} \times 50 \text{ V} = 300 \mu\text{C}$$

$$v_1 = \frac{Q}{C_1} = 20 \text{ V}$$

$$v_2 = \frac{Q}{C_2} = 30 \text{ V}$$

As a check, we verify that $v_1 + v_2 = 50 \text{ V}$.

P3.48 Because we have $v_L(t) = L \frac{di_L(t)}{dt}$, the voltage is zero when the current is constant. Thus, we say that inductors act as short circuits for steady dc currents.

P3.49 $L = 0.1 \text{ H} \quad i_L(t) = 0.5 \sin(1000t) \text{ A}$

$$v_L(t) = L \frac{di_L(t)}{dt} = 50 \cos(1000t) \text{ V}$$

$$p(t) = v_L(t)i_L(t) = 25 \cos(1000t)\sin(1000t) = 12.5 \sin(2000t) \text{ W}$$

$$w(t) = \frac{1}{2} L [i_L(t)]^2 = 0.0125 \sin^2(1000t) \text{ J}$$

The sketches should be similar to the following plots. The units for the quantities in these plots are A, V, W, J and s.

